



Cairo University  
Faculty of Engineering  
Systems and Biomedical Engineering  
Bioelectronics



## Final project


Submitted to:

**Dr.Ahmed Ehab**

Prepared by:

<i>Name</i>	<i>Sec</i>	<i>B.N</i>
Ahmed Mohamed Abdelfatah	1	5
Mohamed Adel Mahmoud	2	16
Miran Mahmoud mabrouk	2	34
Mariam Mohamed Osama	2	25
Rania Atef Omar	1	32

## Block Diagram

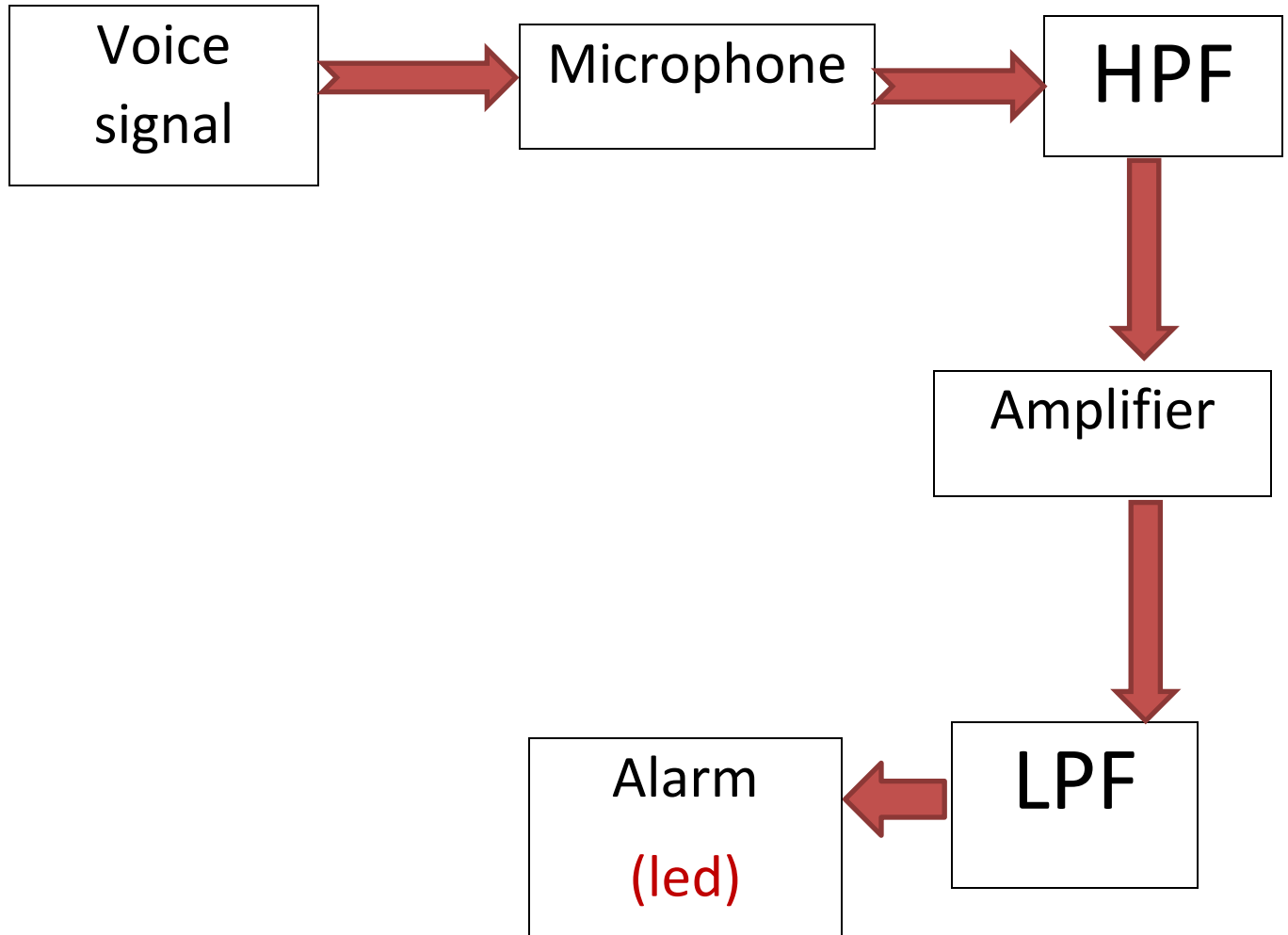

## Description

The output of an electret microphone (hooked up according to its datasheet through a band-pass amplifier based on an LM324 operational amp. the op-amp circuit has both a high-pass portion (R3 AND C1) and a low-pass portion (R4 AND C2). the circuit attenuates frequencies above  $f=1/(2\pi R2C1)=250\text{Hz}$  and frequencies below  $f=1/(2\pi R5C2)=4\text{kHz}$ . the op-amp acts as a non-inverting amplifier with a gain  $(1+(56/1))=57\text{v/v}$  then the system in reality enables a led or an alarm when noise is detected in this frequency band which 250-4000Hz, the noise levels inside and outside **the incubator**.

## circuit design

